

Week 4

Design of Full adder

Carry Propagate Adder (CPA)


- Full adder is an arithmetic logic unit or circuit to add two single digit numbers with Carry-in.
- It is still combinational circuit with inputs Ax and Bx.
- S = Sum (1bit); C-in = Carry in; C-out = Carry Out.
- Adder is also called Ripple Carry Adder (RCA)
- Simplest circuit for an adder and has longest propagation delay that is proportional to the number of the carry bits
- Equation to estimate the propagation delay of an n-bit CPA. Δ_{FAC} and Δ_{FAS} stand for delta time for carry bit and delta time for sum signal propagation delay of a Full Adder (FA)

$$\Delta_{CPA}(n) = [(n-1) * \Delta_{FAC}] + \Delta_{FAS} \quad \text{Eq(2.8)}$$

- Using AND/OR/EOR gate, Δ for AND/OR gate is = 0.1 ns and Δ for EOR = 0.3ns, $\Delta_{FAC} = 0.2\text{ns}$ and $\Delta_{FAS} = 0.3\text{ns}$, as per Eq(2.8)
 - For 8 bit CPA (n=8), the equation to calculate propagation delay is as follows:

$$\Delta_{CPA}(n) = (n - 1)(0.2\text{ns}) + 0.3\text{ns}$$

Block Diagram of Full adder

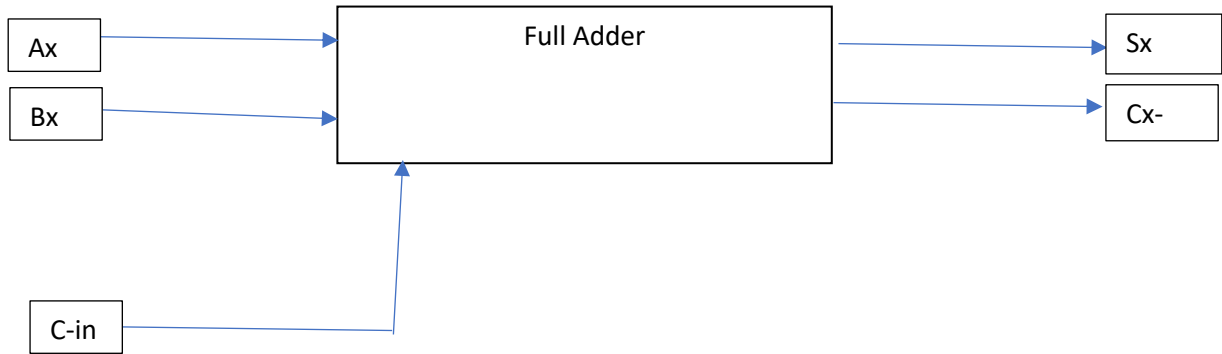


Design of Full Adder

- With three inputs and 2 outputs
- **Full adder Truth Table**

Inputs			Outputs	
A	B	C – IN	Sum	C – Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

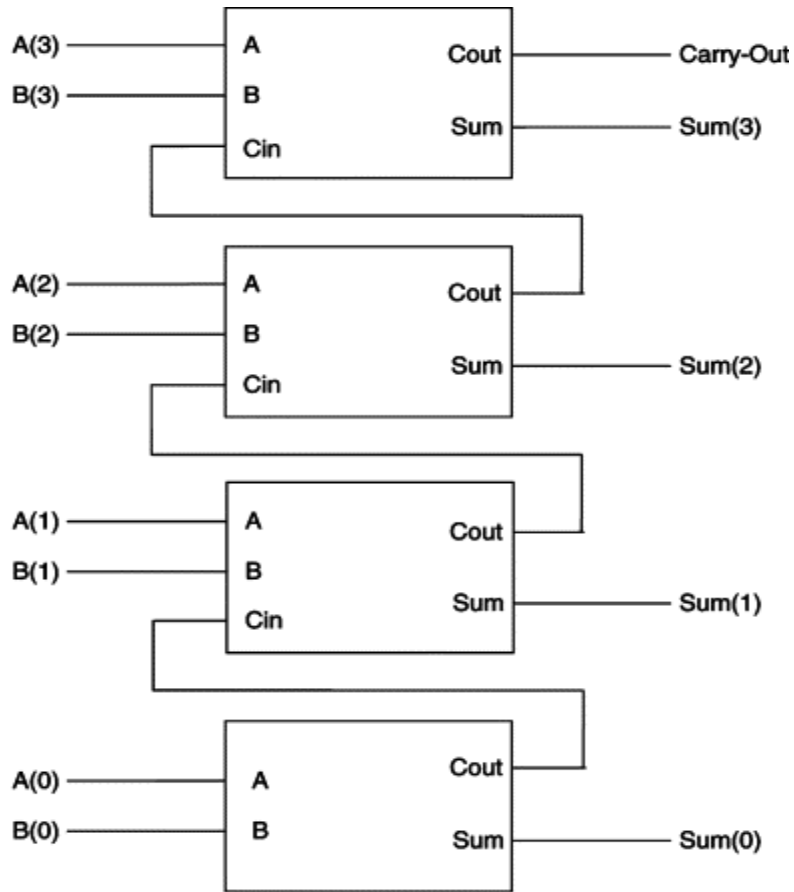Schematic of a 4 bit Carry Propagate Adder (CPA)



4-bit binary addition

	A (3)	A (2)	A (1)	A (0)	
	B (3)	B (2)	B (1)	B (0)	+
<hr/>					
Carry-Out	Sum (3)	Sum (2)	Sum (1)	Sum (0)	
<hr/>					

4-bit binary addition

	A(3)	A(2)	A(1)	A(0)	
	B(3)	B(2)	B(1)	B(0)	+
<hr/>					
Carry-Out	Sum(3)	Sum(2)	Sum(1)	Sum(0)	
<hr/>					

Binary Addition review:

$0 + 0 = 0$; $0 + 1 = 1$; $1 + 0 = 1$;
 $1 + 1 = 10$

A	B	S	Cout
0	0	0	
0	1	1	
1	0	1	
1	1	0	1

A = 0111

B = 1111

Inputs			Output	
A[i]	B[i]	C-in	S	C out
1	1	0	0	1
1	1	1	1	1
1	1	1	1	1
0	1	1	0	1

Week 5

Multiplexer (Mux)

- Selecting of data or information is a critical function in a digital systems and computers
- A Multiplexer (Mux for short) is a digital switch; Mux is a circuit used to select and route any of the several inputs to a output signal
- Mux is a combinational circuit. it has the following:
 - o 2^n inputs
 - o N control inputs
 - o One set of outputs
- For a multiplexer, the value of the control inputs (selector signals) determines the data input that is selected
- Multiplexer means many into one. a simple example of a non-digital circuit of a mux is a single pole multi-position switch. Multi-position switches are widely used in many electronics circuit, however, circuits that operate at high speed require the multiplexer to be automatically selected.
- Example: 1 bit , 2 to 1 Mux
 - o X and Y are the inputs
 - o S is the selector signal
 - o r is the output

Week 5

Design of a 1 bit, 2 to 1 mux

1. Block diagram of 1 bit, 2 to 1 mux

