

Chapter 4


SEQUENTIAL CIRCUITS: CORE MODULES

In this Chapter

- Basic modules for saving sequential circuit's state
 - Latches and flip flops
- Timing constraints
- Other flip-flops
- HDL models

Sequential Circuit Example

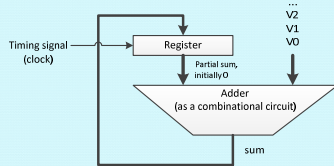
- Register retains state of circuit as *sum*
- Adder computes next *sum* (circuit's next state)
- Timing signal must guarantee *sum* is computed before register loading



SR latch core circuit

- Three basic functions:
 - retain previous value (keeps q as is)
 - store 0 (reset q)
 - store 1 (set q)
- However, four possible cases, only three used
 - $s = 0$ and $r = 0$, retain q
 - $s = 0$ and $r = 1$, reset
 - $s = 1$ and $r = 1$, set
 - $s = 1$ and $r = 1$, not used
 - makes $q = \bar{q}$, invalid
 - causes q and \bar{q} oscillate when both s and r instantly become 0 next

s	r	q^{n+1}
0	0	q^n
0	1	0
1	0	1
1	1	—

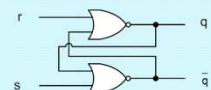


(a)

(b)


SR Latch (added clock signal)

- Goal: Prevent Case 4 ($s = 1$ and $r = 1$ affecting core circuit)
- Includes a signal gating logic to time sampling of inputs (s and r)
 - Only when both s and r are both stable (not changing) should affect core circuit
- Naming convention
 - positive-level, inputs are sampled when $clk = 1$
 - negative-level, inputs are sampled when $clk = 0$
- Assume positive-level (figure below)
 - $clk = 0$, core retains q value
 - $clk = 1$, s and r gated (sampled), enter the core
 - Timing constraint: s and r must stabilize at or before clk changes to 1 (sampling level)
 - s and r called synchronous inputs

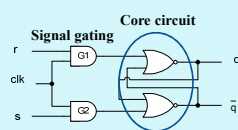


Asynchronous Inputs

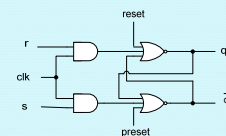- Function: Changes q and \bar{q} independent of clk
- Used for circuit initialization during startup



SR latch, NAND
Version
And
Symbol

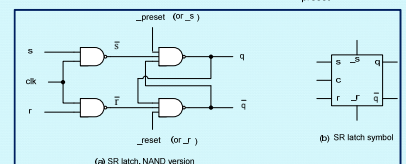


(a) SR latch, NAND version

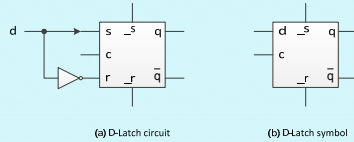(b) SR latch symbol


D Latch

- Requires one (synchronous) input d instead of two in SR latch
- Reduces number of signal routing wires, saves space
- Timing constraint: d must stabilize before clk changes to 1





Disadvantage of Latches

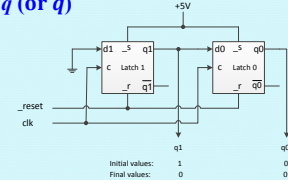- Signal chasing problem
 - Input $d1$ can change values of both $q1$ and $q0$ during the same clk cycle
 - $d1$ should only affect $q1$
- Limited application: Cannot be used to design circuits when d depends on a q (or \bar{q})
 - E.g., shift register





D Flip-Flop

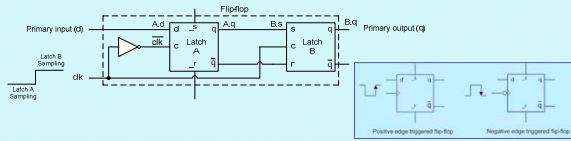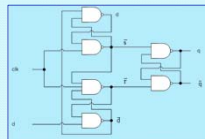- No signal chasing problem
- Can use two latches, one positive-level and one negative-level
 - The two latches act like "double-door entry"
- Called edge triggered, d sampled at clk edge
 - Positive edge when clk makes 0-1 transition
 - Negative edge when clk makes 1-0 transition
- Timing constraint: d must remain stable before and after the sampling clk edge




Setup and Hold times

 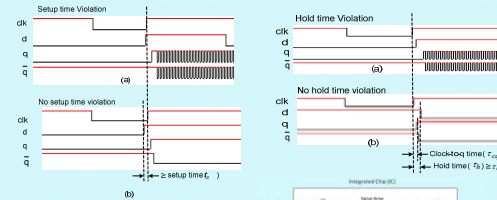- Set-up time: Minimum time d must be stable before clk sampling edge
- Hold time: Minimum time d must remain stable after clk sampling edge
 - May be negative due to difference in d and clk wire delays



Clock Frequency Estimation – Without Clock Skew

 
Minimum clock frequency, not including wire delays



$$\tau \geq \tau_{cq-max} + \tau_{pd-max} + \tau_s \quad f \leq \frac{1}{\tau} \text{ cycles/sec or Hertz}$$


D Flip-Flop with Enable

 - Retains q when $e = 0$
- Used when one or more flip-flops selected among many



Other flip-flops

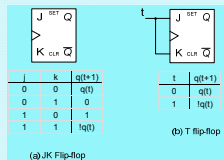- **JK flip-flop**
 - Uses two inputs called j and k
 - $j = k = 1$ will not cause oscillation
 - Better when wires require less space than gates
 - Not necessarily true today
- **T (toggle) flip-flop**
 - q alternates every clock cycle when $t = 1$
 - E.g., consider when $t = 1$, q controls a 2-to-1 MUX
- Both can be designed to operate edge triggered



D Latch HDL Model (Behavioral)

```

module d_latch
(
    input clock, _reset, _preset, d,
    output reg q,
    output nq
);

    assign nq = ~q;

    always@(clock or !_reset or !_preset or d)    Designed like a combinational circuit.
    begin
        if(!_reset)
            q <= 0;
        else if(!_preset)
            q <= 1;
        else if(clock)
            q <= d;    Except, note the missing else here
                        (creates a D-latch)
    end
endmodule

    "==" called non-blocking or concurrent assignment
  
```

D flip-flop HDL Model (Behavioral)

```

module dff
(
    input clock, _reset, _preset, d, e,
    output reg q,
    output nq
);

    assign nq = ~q;

    always@(posedge clock, _reset, _preset)    Note the missing synchronous inputs
    begin                                     d and e here
        if(!_reset)
            q <= 0;
        else if(!_preset)
            q <= 1;
        else if(e)
            q <= d;    Note also the missing else here
                        (creates a D flip-flop)
    end
endmodule
  
```