

Seq Circuit : Single Cycle

- Equation Estimates min clock period req. to run the data path.

$$T \geq 2 \Delta_{Add} + \Delta_{Add/Sub} + T_{st} + T_{ca} + T_{cs} \quad (Eq 6.1)$$

- Data path that computes either the quantity $A + B + C + D$ or $A + B + C - D$

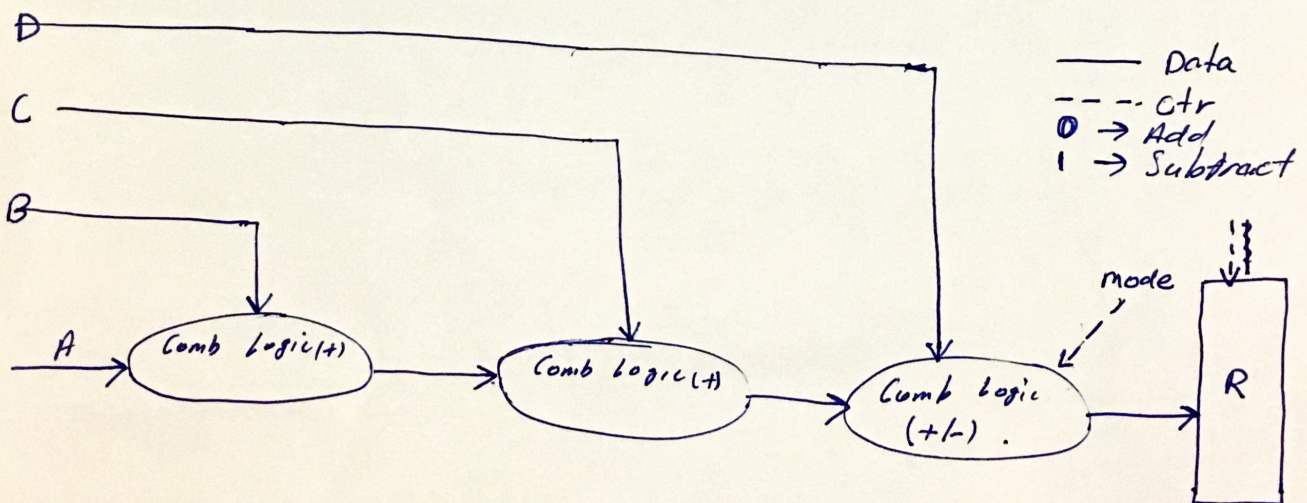


Fig 6.2 : Single Cycle two function data path - one clock cycle. Register

Seq Circuit : multicycle

- A multicycle data path requires that a computation be divided and computed in steps - simple datapath.
- A multicycle algorithm to implement $R \leftarrow A + B + C \pm D$ (5 possible simple operations)
 - cycle 1: $R \leftarrow A$
 - cycle 2: $R \leftarrow R + B$
 - cycle 3: $R \leftarrow R + C$
 - cycle 4: if $mode == 0$ then $R \leftarrow R + D$; otherwise $R \leftarrow R - D$
- Clock period of a multicycle data path is also proportional to longest signal path.

$$T = \Delta_{mux1} + \Delta_{Add/Sub} + \Delta_{mux2} + T_{st} + T_{cq} + T_{cs}$$

 


Fig 6.2

Fig 6.3: multicycle data - Requiring 4 Cycles

Seq Circuit: Pipelined Data Path (Cont)

- Computing stream of quantities $A_i + B_i + C_i \pm D_i$

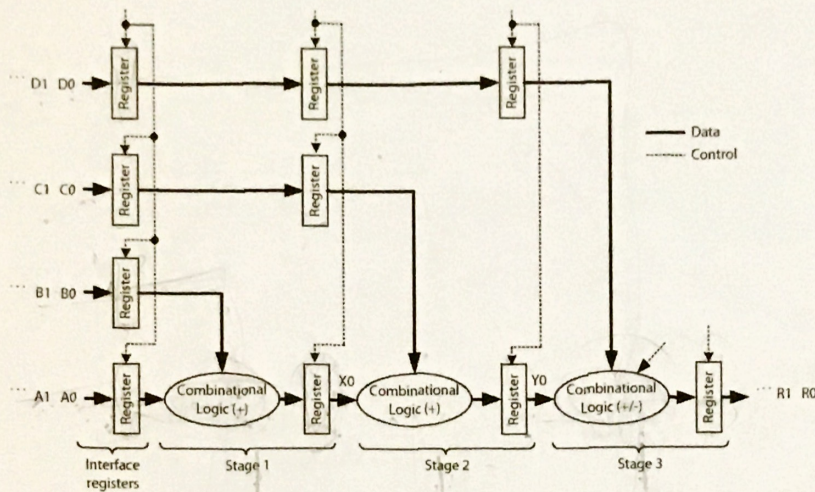


FIGURE 6.4 A two-function pipelined data path computing a stream of quantities $A_i + B_i + C_i \pm D_i$ for $i = 0, 1, 2$, etc.