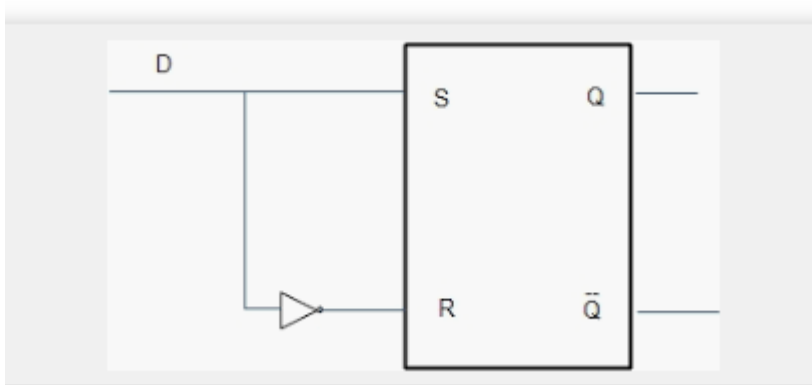


## Sequential Circuit – Core modules

- Latches are basic building block of flip-flops (Basic memory Unit).
- Two types of memory elements based on the type of trigger that is suitable to operate
  - Latches
  - Flip Flops
- Latches operate with enable signal, which is level sensitive, where as flip-flops are edge sensitive.

### ***D flip-flop***

- Basic memory storage device.
- For D flip-flop, a clock signal is needed to change states.
- D flip flop is designed using S-R latches.
- Similar to S-R latch, only we use set and reset function. (Tie D input to s input and not D to R input to make S\_R flip flop into D flip flop.
- Block Diagram of D flip flop.



## Sequential Circuit: Core Modules (Cont)

Internal circuit of D flip flop:

